



# MACHAKOS UNIVERSITY

University Examinations for 2022/2023 Academic Year

SCHOOL OF ENGINEERING AND TECHNOLOGY

DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING

THIRD YEAR FIRST SEMESTER EXAMINATION FOR

BACHELOR OF SCIENCE (ELECTRICAL AND ELECTRONIC ENGINEERING)

EEE 308: ANALOGUE ELECTRONICS I

DATE:

TIME:

---

## INSTRUCTIONS

Answer question **ONE** and **ANY OTHER TWO** questions

### QUESTION ONE (COMPULSORY) (30 MARKS)

- a) Calculate the dynamic forward and reverse resistance of a PN junction Germanium diode, given that the applied voltage is 0.25 V,  $I_o = 1 \mu\text{A}$  and  $T = 300^\circ \text{K}$ . (6 marks)
- b) Derive the relationship between base current amplification factor  $\beta$  and emitter current amplification factor  $\alpha$ . (6 marks)
- c) The measured values of a diode at a junction temperature of  $27^\circ\text{C}$  are given by


$$V_D = \begin{cases} 0.5 \text{ V} & \text{at } I_D = 5 \mu\text{A} \\ 0.6 \text{ V} & \text{at } I_D = 100 \mu\text{A} \end{cases}$$

Determine

- i. the emission coefficient  $\eta$  and  
ii. the leakage current  $I_S$ .

(6 marks)

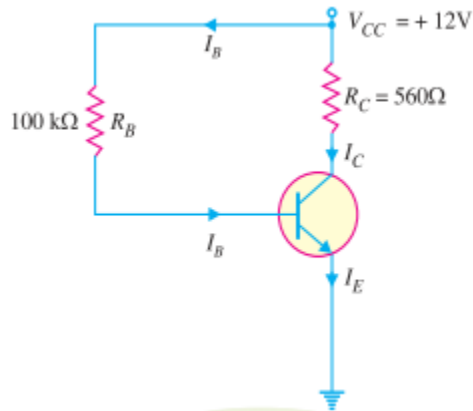
- d) A base resistor bias circuit in FigQ1 (d) is subjected to an increase in temperature from 25°C to 75°C. If  $\beta = 100$  at 25°C and 150 at 75°C, determine the percentage change in Q-point values ( $V_{CE}$  and  $I_C$ ) over this temperature range. Neglect any change in  $V_{BE}$  and the effects of any leakage current.



**FigQ1 (d)**

(8 marks)

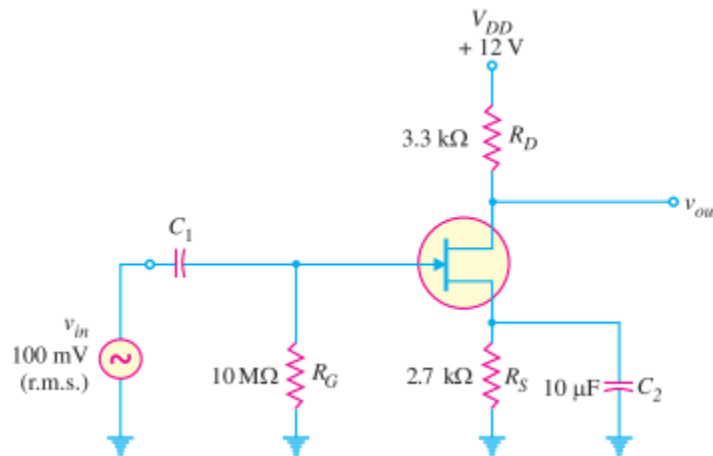- e) What is the r.m.s. output voltage of the unloaded amplifier in FigQ1 (e) given that  $I_{DSS} = 8$  mA,  $V_{GS(off)} = -10$  V and  $I_D = 1.9$  mA?



**FigQ1 (e)**

(4 marks)

### QUESTION TWO (20 MARKS)

- a) An NPN transistor with  $\beta = 50$ , is used in Common Emitter circuit with  $V_{CC} = 10V$  and  $R_C = 2\text{ k}\Omega$ . The bias is obtained by connecting a  $100\text{ k}\Omega$  resistance from collector to base. Assume  $V_{BE} = 0\text{ V}$ . Find
- The Quiescent Point;
  - The Stability Factor.
- (4 marks)
- b) One NPN transistor is used in the potential divider biasing arrangement. The circuit components values are  $V_{CC} = 4.5V$ ,  $R_C = 1.5\text{ k}\Omega$ ,  $R_E = 0.27\text{ k}\Omega$ ,  $R_2 = 2.7\text{ k}\Omega$  and  $R_1 = 27\text{ k}\Omega$ . If  $\beta = 44$ . Find the
- Stability Factor;
  - Quiescent point Q.
- (4 marks)
- c) Derive the expression for stability factor S for potential divider method of biasing.
- (8 marks)

### QUESTION THREE (20 MARKS)

- a) Given that  $V_{CC} = +12\text{ V}$ ,  $R_B = 240\text{ k}\Omega$  and  $R_C = 2.2\text{ k}\Omega$  determine the following for a common emitter transistor using fixed bias configuration
- $I_{BQ}$  and  $I_{CQ}$ ;
  - $V_{CEQ}$ ;
  - $V_B$  and  $V_C$ ;
  - $V_{BC}$ .
- (6 marks)
- b) For the network of Fig.Q4 (b)
- Determine  $I_{CQ}$  and  $V_{CEQ}$ ;

- ii. Find  $V_B$ ,  $V_C$ ,  $V_E$  and  $V_{BC}$ .

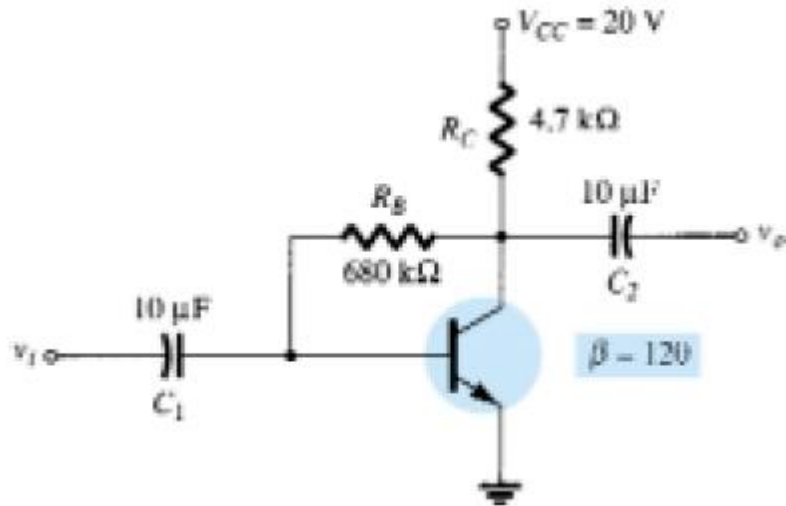


Fig.Q4 (b)

- c) Determine the dc bias voltage  $V_{CE}$  and the current  $I_C$  for CE amplifier using the voltage-divider configuration and having the following parameters:  $V_{CC} = +22\text{ V}$ ,  $R_C = 10\text{ k}\Omega$ ,  $R_E = 1.5\text{ k}\Omega$ ,  $R_2 = 3.9\text{ k}\Omega$  and  $R_1 = 39\text{ k}\Omega$  and  $\beta = 140$ .

(7 marks)


(7 marks)

#### QUESTION FOUR (20 MARKS)

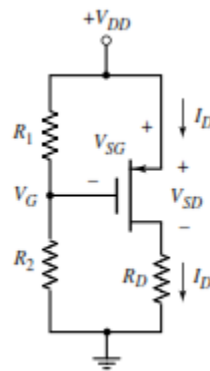- a) FigQ4 (a) shows a p-channel enhancement-mode MOSFET circuit. Calculate

- the drain current  $I_D$ ;
- source-to-drain voltage  $V_{SD}$ .


Assume that  $R_1 = R_2 = 50\text{ k}\Omega$ ,  $V_{DD} = 5\text{ V}$ ,  $R_D = 7.5\text{ k}\Omega$ ,  $V_{TP} = -0.8\text{ v}$ , and  $K_p = 0.2\text{ mA/V}^2$ .



FigQ4 (a)

(10 marks)

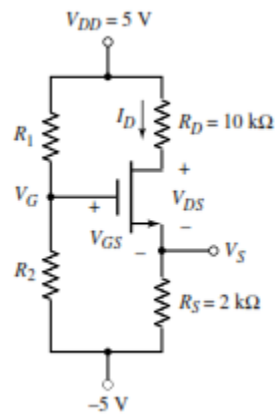- (b) For the dc circuit in FigQ4 (b), assume that the MOSFET parameters are  $V_{TN} = 2 \text{ V}$ ,  $k'_n = 80 \mu\text{A}/\text{V}^2$ , and  $W/L = 4$ . Choose  $R_1$  and  $R_2$  such that the current in the bias resistors is approximately one-tenth of  $I_D$ . Design the circuit such that  $I_D = 0.5 \text{ mA}$ .



FigQ4 (b)

(10 marks)

**QUESTION FIVE (20 MARKS)**

- a) Determine the following for the network in Fig.Q5 (a)
- i.  $I_{DQ}$  and  $V_{GSQ}$ ;
  - ii.  $V_D$ .

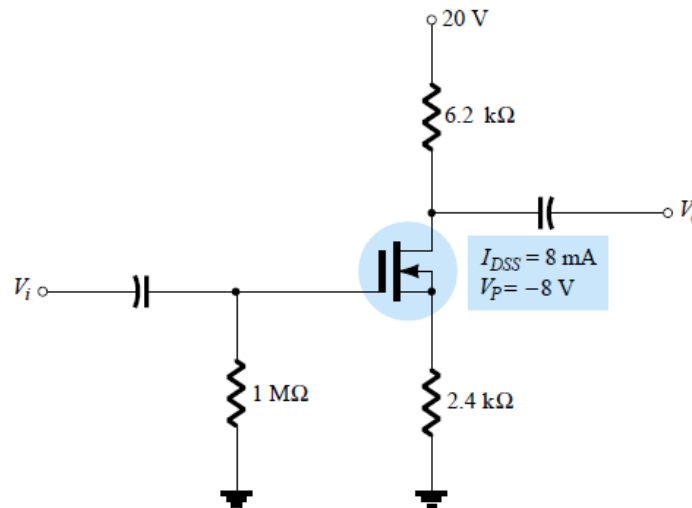


Fig.Q5 (a)

(8 marks)

b) The following readings were obtained experimentally from a JFET:

$V_{GS}$	0V	0 V	- 0.2 V
$V_{DS}$	7 V	15 V	15 V
$I_D$	10 mA	10.25 mA	9.65 mA

Determine

- i. A.C. drain resistance;
- ii. Trans-conductance;
- iii. Amplification factor.

(8 marks)

c) In an n-channel JFET biased by potential divider method, it is desired to set the operating point at  $I_D = 2.5$  mA and  $V_{DS} = 8$  V. If  $V_{DD} = 30$  V,  $R_1 = 1$  M $\Omega$  and  $R_2 = 500$  k $\Omega$ , find the value of  $R_S$ . The parameters of JFET are  $I_{DSS} = 10$  mA and  $V_{GS(off)} = - 5$  V.

(4 marks)